

Nano-Ampere Meter

RAJU BADDI

May 1, 2011



This circuit can measure currents down into the nano-ampere range. It is useful when building, testing and experimenting with low-power circuits, especially those operating off batteries.

The circuit is built around commonly available JFET input op-amp TL081 and a few precision resistors. It has a wide operating range from 0-10 nA to 0-1 A in steps of multiplicative decades. the range can be easily extended to 10 A and 100 A by including additional range resistors of 100 ohms respectively.

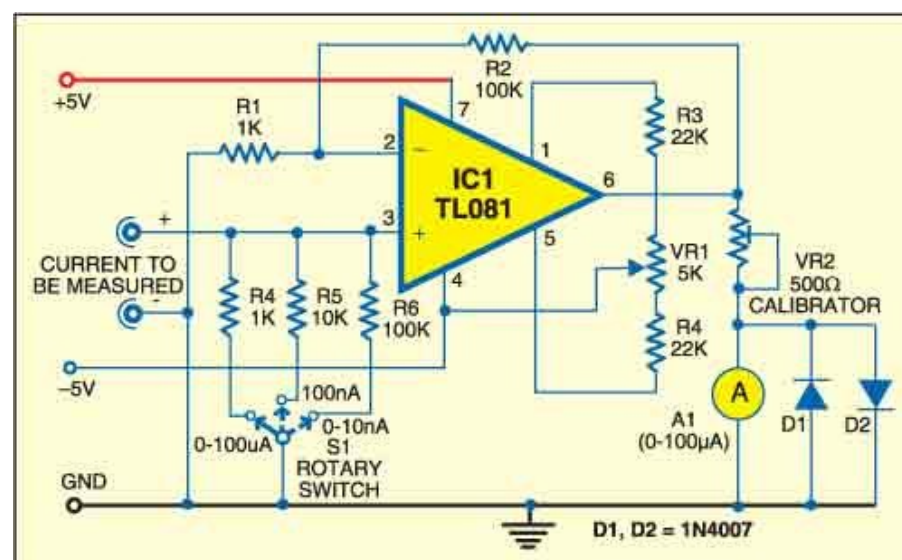
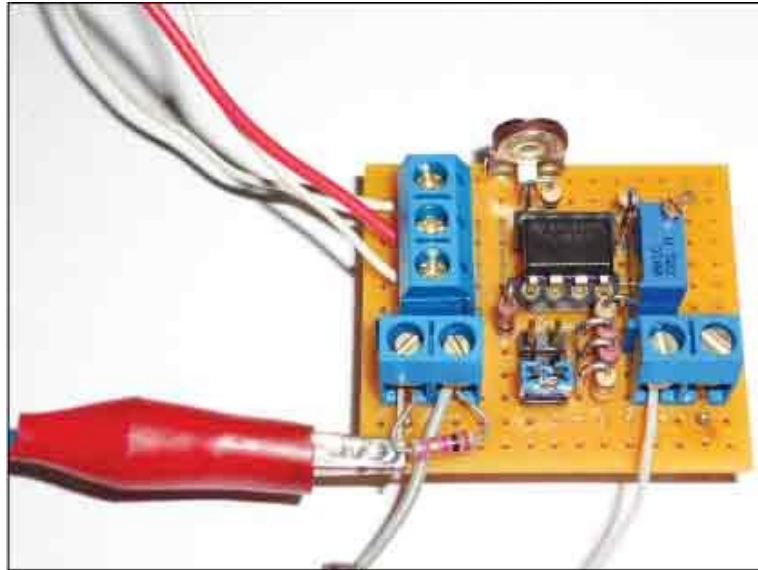


Fig. 1: Circuit of nano-ampere meter

The $\pm 5V$ supply (not shown in the circuit) may be obtained from standard regulators to power the circuit. IC TL081 is wired as a high-gain non-inverting amplifier with a gain of $R_f / R_1 + 1 = 100$. The current to be measured is passed through a resistor. The voltage drop across this resistor is applied to the amplifier input. The output voltage is $100 \times I_m \times R$ (where I_m is the current to be measured). The range can be controlled by changing R (1 kohms, 10 kohms and 100 kohms) appropriately.

*Fig. 2: Author's prototype*

The diode in parallel with the meter protects the circuit against high currents due to improper range selection. Further, the range resistors do not have any effect on the current to be measured. For instance, to produce a current of 1 μA source, it is necessary to include a 500-mega-ohm resistor in the circuit. Since the circuit is being used to sample this current, it is very small as compared to the large value of the range resistors.

Any meter can be used to calibrate the output, provided the gain of the amplifier is changed appropriately. That is, a meter with full-scale deflection of 150 μA would require a gain of 150 and vice-versa. Using a commonly available digital multimeter, adjust the preset VR2 such that the resistance of the calibrator and 100 μA meter (typical resistance of 700 ohms) in series is exactly 1 kilo-ohm. Now wire the entire circuit to the set-zero trimpot to get zero deflection in any range of the multimeter. The nano-ampere meter is ready for use.

Assemble the circuit on a general-purpose PCB and enclose it in a small case. Provide a meter on the front panel. Provide three terminals for the power supply.

GND) on the rear panel and two terminals on the front panel for the current to
